

Find the Norton equivalent with respect to terminals *a* and *b* for the circuit shown.

$I_N =$ _____

$R =$ _____

