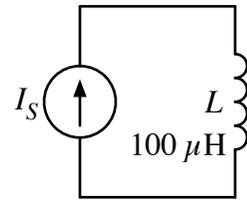


A time-varying current source is connected to a 100- μH inductor. The source has the following time-dependence:



For $0 < t \leq 25 \mu\text{s}$, the current increases linearly:

$$I_S(t) = (2 \times 10^5 \text{ A/s}) \cdot t$$

For $25 \mu\text{s} < t \leq 100 \mu\text{s}$, the current decreases linearly:

$$I_S(t) = 5 \text{ A} - (6.67 \times 10^4 \text{ A/s}) (t - 25 \mu\text{s})$$

For $100 \mu\text{s} < t \leq 150 \mu\text{s}$, the current increases parabolically:

$$I_S(t) = 5 \text{ A} - (2 \times 10^9 \text{ A/s}^2) (t - 150 \mu\text{s})^2$$

For $150 \mu\text{s} < t \leq 200 \mu\text{s}$, the current decreases parabolically:

$$I_S(t) = (2 \times 10^9 \text{ A/s}^2) (t - 200 \mu\text{s})^2$$

