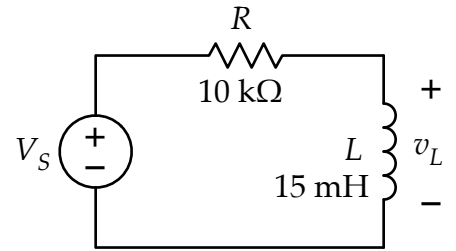
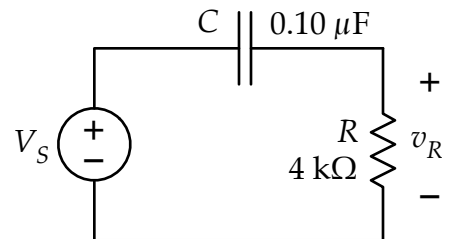


a. In the circuit at right,  $V_s = (8V)\cos\omega t$ . Find the frequency ( $f$  not  $\omega$ ) for which the *magnitude* of  $v_L$  is 2 V. Calculate the phase of  $v_L$  at that frequency.



$f =$  \_\_\_\_\_  $\theta_L =$  \_\_\_\_\_

b. In the circuit at right  $V_s = (8V)\cos\omega t$ . Find the frequency ( $f$  not  $\omega$ ) for which the *phase* of  $v_R$  is  $+45^\circ$ . Calculate the magnitude of  $v_R$  at that frequency.



$f =$  \_\_\_\_\_  $|\tilde{\mathbf{V}}_R| =$  \_\_\_\_\_